



TaaviSalum Small error fix at exercise 4 ...

18 seconds ago  History

..



Pictures

4 minutes ago



flip_flops

4 minutes ago



README.md

18 seconds ago



README.md

Digital-electronics-1

Laboratory #7

Exercise 1: Preparation tasks

D-type flip-flop equation and truth table

$$q_{n+1}^D = d$$

clk	d	q(n)	q(n+1)	Comments
↑	0	0	0	Remembers values, no change
↑	0	1	0	Remembers values, no change
↑	1	0	1	Sampled and stored

clk	d	q(n)	q(n+1)	Comments
↑	1	1	1	Sampled and stored

JK-type flip-flop equation and truth table

$$q_{n+1}^{JK} = j \cdot \overline{q_n} + \overline{k} \cdot q_n$$

clk	j	k	q(n)	q(n+1)	Comments
↑	0	0	0	0	No change
↑	0	0	1	1	No change
↑	0	1	0	0	Reset
↑	0	1	1	0	Reset
↑	1	0	0	1	Set
↑	1	0	1	1	Set
↑	1	1	0	1	Toggle (Invert)
↑	1	1	1	0	Toggle (Invert)

T-type flip-flop equation and truth table

$$q_{n+1}^T = t \cdot \overline{q_n} + \overline{t} \cdot q_n$$

clk	t	q(n)	q(n+1)	Comments
↑	0	0	0	No change
↑	0	1	1	No change
↑	1	0	1	Invert (Toggle)
↑	1	1	0	Invert (Toggle)

Exercise 2: D latch

VHDL code of the process `p_d_latch` :

```

p_d_latch : process (en, d, arst)
begin
    if (arst = '1') then
        q      <= '0';
        q_bar  <= '1';
    elsif (en = '1') then
        q      <= d;
        q_bar  <= not d;
    end if;
end process p_d_latch;

```

VHDL testbench file `tb_d_latch` :

```

-----
-- Reset generation process
-----

```

```

p_reset_gen : process
begin
    s_arst <= '0';
    wait for 152 ns;
    s_arst <= '1'; -- Reset
    wait for 212 ns;
    s_arst <= '0';
    wait for 320 ns;
    s_arst <= '1'; -- Reset
    wait;
end process p_reset_gen;

```

```

-----
-- Data generation process
-----

```

```

p_stimulus : process
begin
    report "Stimulus process started" severity note;

    s_en <= '0';
    s_d  <= '0';
    wait for 40 ns;
    s_d  <= '1';
    wait for 40 ns;
    s_d  <= '0';
    wait for 40 ns;
    s_d  <= '1';
    wait for 40 ns;
    s_d  <= '0';
    wait for 20 ns;

    assert ((s_arst = '1') and (s_en = '0') and (s_q = '0') and (s_q_bar = '1'

```

```
report "Test failed when RESET is '1', EN is '0' and D is '0'" severity error

wait for 20 ns;
s_d <= '1';
wait for 20 ns;

assert ((s_arst = '1') and (s_en = '0') and (s_q = '0') and (s_q_bar = '1'))
report "Test failed when RESET is '1', EN is '0' and D is '1'" severity error

wait for 20 ns;
s_d <= '0';
s_en <= '1';
wait for 40 ns;
s_d <= '1';
wait for 20 ns;

assert ((s_arst = '1') and (s_en = '1') and (s_q = '0') and (s_q_bar = '1'))
report "Test failed when RESET is '1', EN is '1' and D is '1'" severity error

wait for 20 ns;
s_d <= '0';
wait for 20 ns;

assert ((s_arst = '1') and (s_en = '1') and (s_q = '0') and (s_q_bar = '1'))
report "Test failed when RESET is '1', EN is '1' and D is '0'" severity error

wait for 20 ns;
s_d <= '1';
wait for 40 ns;
s_d <= '0';
wait for 40 ns;
s_d <= '1';
wait for 20 ns;

assert ((s_arst = '0') and (s_en = '1') and (s_q = '1') and (s_q_bar = '0'))
report "Test failed when RESET is '0', EN is '1' and D is '1'" severity error

wait for 60 ns;
s_d <= '0';
wait for 20 ns;

assert ((s_arst = '0') and (s_en = '1') and (s_q = '0') and (s_q_bar = '1'))
report "Test failed when RESET is '0', EN is '1' and D is '0'" severity error

wait for 20 ns;
s_d <= '1';
wait for 20 ns;
s_en <= '0';
wait for 20 ns;
s_d <= '0';
wait for 40 ns;
```

```

s_d  <= '1';
wait for 40 ns;
s_d  <= '0';
wait for 40 ns;
s_d  <= '1';
wait for 40 ns;
s_d  <= '0';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Simulated time waveforms



Exercise 3: Flip-flops

VHDL code of the process p_d_ff_arst :

```

p_d_ff_arst : process (clk, arst)
begin
    if (arst = '1') then
        q      <= '0';
        q_bar <= '1';
    elsif rising_edge(clk) then
        q      <= d;
        q_bar <= not d;
    end if;
end process p_d_ff_arst;

```

VHDL testbench file tb_d_ff_arst :

```

-----
-- Clock generation process
-----

p_clk_gen : process
begin
    while now < 40 ms loop

```

```

        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----

-- Reset generation process
-----

p_reset_gen : process
begin
    s_arst <= '0';
    wait for 28 ns;
    s_arst <= '1'; -- Reset
    wait for 13 ns;
    s_arst <= '0';
    wait for 17 ns;
    s_arst <= '1';
    wait for 693 ns;
    s_arst <= '1'; -- Reset
    wait;
end process p_reset_gen;

-----

-- Data generation process
-----

p_stimulus : process
begin
    report "Stimulus process started" severity note;

    s_d <= '0';
    wait for 14 ns;
    s_d <= '1';
    wait for 2 ns;

    assert ((s_arst = '0') and (s_q = '1') and (s_q_bar = '0'))
    report "Test failed when RESET is '0', CLK is RISING and D is '1'" sever

    wait for 8 ns;
    s_d <= '0';
    wait for 10 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
    wait for 10 ns;
    s_d <= '1';
    wait for 5 ns;

```

```

assert ((s_arst = '1') and (s_q = '0') and (s_q_bar = '1'))
report "Test failed when RESET is '1', CLK is FALLING and D is '1'" severity error;

wait for 5 ns;
s_d <= '0';
wait for 14 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Simulated time waveforms



VHDL code of the process p_d_ff_rst :

```

p_d_ff_rst : process (clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            q      <= '0';
            q_bar <= '1';
        else
            q      <= d;
            q_bar <= not d;
        end if;
    end if;
end process p_d_ff_rst;

```

VHDL testbench file tb_d_ff_rst :

```
-----  
-- Clock generation process  
-----  
    p_clk_gen : process  
    begin  
        while now < 40 ms loop  
            s_clk_100MHz <= '0';  
            wait for c_CLK_100MHZ_PERIOD / 2;  
            s_clk_100MHz <= '1';  
            wait for c_CLK_100MHZ_PERIOD / 2;  
        end loop;  
        wait;  
    end process p_clk_gen;  
  
-----  
-- Reset generation process  
-----  
  
    p_reset_gen : process  
    begin  
        s_rst <= '0';  
        wait for 28 ns;  
        s_rst <= '1'; -- Reset  
        wait for 13 ns;  
        s_rst <= '0';  
        wait for 17 ns;  
        s_rst <= '1'; -- Reset  
        wait for 693 ns;  
        s_rst <= '1'; -- Reset  
        wait;  
    end process p_reset_gen;  
  
-----  
-- Data generation process  
-----  
  
    p_stimulus : process  
    begin  
        report "Stimulus process started" severity note;  
  
        s_d <= '0';  
        wait for 14 ns;  
        s_d <= '1';  
        wait for 2 ns;  
  
        assert ((s_rst = '0') and (s_q = '1') and (s_q_bar = '0'))  
        report "Test failed when RESET is '0', CLK is RISING and D is '1'" severity  
  
        wait for 8 ns;  
        s_d <= '0';  
        wait for 10 ns;
```



```

s_d  <= '1';
wait for 10 ns;
s_d  <= '0';
wait for 10 ns;
s_d  <= '1';
wait for 5 ns;


assert ((s_rst = '1') and (s_q = '1') and (s_q_bar = '0'))
report "Test failed when RESET is '1', CLK is FALLING and D is '1'" severity

wait for 5 ns;
s_d  <= '0';
wait for 14 ns;
s_d  <= '1';
wait for 10 ns;
s_d  <= '0';
wait for 10 ns;
s_d  <= '1';
wait for 10 ns;
s_d  <= '0';
wait for 10 ns;
s_d  <= '1';
wait for 10 ns;
s_d  <= '0';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Simulated time waveforms

 

VHDL code of the process p_jk_ff_rst :

```

p_jk_ff_rst : process (clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            s_q <= '0';
        else
            if (j = '0' AND k = '0') then
                s_q <= s_q;
            elsif (j = '0' AND k = '1') then

```

```

        s_q <= '0';
    elsif (j = '1' AND k = '0') then
        s_q <= '1';
    elsif (j = '1' AND k = '1') then
        s_q <= not s_q;
    end if;
end if;
end if;
end process p_jk_ff_rst;

q <= s_q;
q_bar <= not s_q;

```

VHDL testbench file tb_jk_ff_rst :

```

-----
-- Clock generation process
-----

```

```

p_clk_gen : process
begin
    while now < 40 ms loop
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

```

```

-----
-- Reset generation process
-----

```

```

p_reset_gen : process
begin
    s_rst <= '0';
    wait for 18 ns;
    s_rst <= '1'; -- Reset
    wait for 13 ns;
    s_rst <= '0';
    wait for 47 ns;
    s_rst <= '1'; -- Reset
    wait for 693 ns;
    s_rst <= '1'; -- Reset
    wait;
end process p_reset_gen;

```

```

-----
-- Data generation process

```

```
-----
p_stimulus : process
begin
    report "Stimulus process started" severity note;

    s_j <= '0';
    s_k <= '0';
    wait for 38 ns;

    assert ((s_rst = '0') and (s_j = '0') and (s_k = '0') and (s_q = '0') and
    report "Test failed when RESET is '0', CLK is RISING, J is '0' and K is '

    wait for 2 ns;
    s_j <= '1';
    s_k <= '0';
    wait for 6 ns;

    assert ((s_rst = '0') and (s_j = '1') and (s_k = '0') and (s_q = '1') and
    report "Test failed when RESET is '0', CLK is RISING, J is '1' and K is '

    wait for 1 ns;
    s_j <= '0';
    s_k <= '1';
    wait for 13 ns;

    assert ((s_rst = '0') and (s_j = '0') and (s_k = '1') and (s_q = '0') and
    report "Test failed when RESET is '0', CLK is RISING, J is '0' and K is '

    wait for 1 ns;
    s_j <= '1';
    s_k <= '0';
    wait for 7 ns;
    s_j <= '1';
    s_k <= '1';
    wait for 8 ns;

    assert ((s_rst = '0') and (s_j = '1') and (s_k = '1') and (s_q = '0') and
    report "Test failed when RESET is '0', CLK is RISING, J is '1' and K is '


    wait for 2 ns;
    s_j <= '0';
    s_k <= '0';
    wait for 7 ns;
    s_j <= '0';
    s_k <= '1';
    wait for 7 ns;
    s_j <= '1';
    s_k <= '0';
    wait for 7 ns;
    s_j <= '1';
    s_k <= '1';
```

```

        report "Stimulus process finished" severity note;
        wait;
    end process p_stimulus;

```

Simulated time waveforms

 

VHDL code of the process p_t_ff_rst :

```

p_t_ff_rst : process (clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            s_q <= '0';
        elsif (t = '1') then
            s_q <= not s_q;
        end if;
    end if;
end process p_t_ff_rst;

q <= s_q;
q_bar <= not s_q;

```

VHDL testbench file tb_t_ff_rst :

```

-----
-- Clock generation process
-----

p_clk_gen : process
begin
    while now < 40 ms loop
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

```

```
-----
-- Reset generation process
-----
```

```
p_reset_gen : process
begin
    s_rst <= '0';
    wait for 18 ns;
    s_rst <= '1'; -- Reset
    wait for 13 ns;
    s_rst <= '0';
    wait for 47 ns;
    s_rst <= '1'; -- Reset
    wait for 693 ns;
    s_rst <= '1'; -- Reset
    wait;
end process p_reset_gen;
```

```
-----
-- Data generation process
-----
```

```
p_stimulus : process
begin
    report "Stimulus process started" severity note;

    s_t <= '0';
    wait for 38 ns;

    assert ((s_rst = '0') and (s_t = '0') and (s_q = '0') and (s_q_bar = '1'))
    report "Test failed when RESET is '0', CLK is RISING and T is '0'" severity error;

    wait for 2 ns;
    s_t <= '1';
    wait for 6 ns;

    assert ((s_rst = '0') and (s_t = '1') and (s_q = '1') and (s_q_bar = '0'))
    report "Test failed when RESET is '0', CLK is RISING and T is '1'" severity error;

    wait for 1 ns;
    s_t <= '0';
    wait for 13 ns;

    assert ((s_rst = '0') and (s_t = '0') and (s_q = '1') and (s_q_bar = '0'))
    report "Test failed when RESET is '0', CLK is RISING and T is '0'" severity error;

    wait for 1 ns;
    s_t <= '1';
    wait for 5 ns;

    assert ((s_rst = '0') and (s_t = '1') and (s_q = '0') and (s_q_bar = '1'))
    report "Test failed when RESET is '0', CLK is RISING and T is '1'" severity error;
```


```

wait for 12 ns;
s_t  <= '0';
wait for 7 ns;
s_t  <= '1';
wait for 7 ns;
s_t  <= '0';
wait for 7 ns;
s_t  <= '1';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Simulated time waveforms

 

Exercise 4: Shift register schematic

Sketch of the shift register schematic:

